

Chapter-6

Combinational logic Design :-


- Analysis
- Design

Steps of Design :-

1. Problem statement
2. Truth Table
3. K-map
4. Logic Diagram

Step-1:

A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

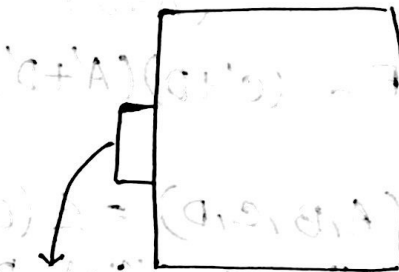


Output
X
Door open: 1
Door close: 0

Absent: 0
Present: 1

Condition S: (to open door)


- (1) If A is absent,
B, C, D should be present
- (2) If A is present,
B, C, D এর atleast একজনকে
present থাকতে হবে

Step-2:

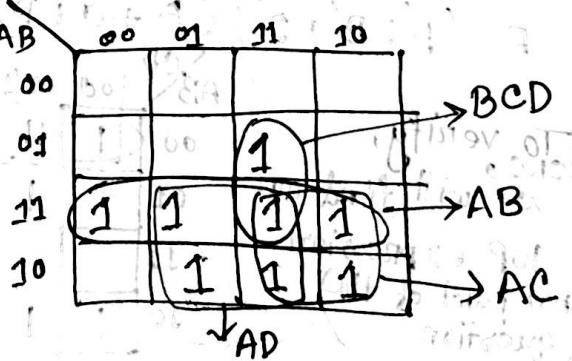


$$X = AB + AD + AC + BCD$$

Step-3: Logic Diagram:-

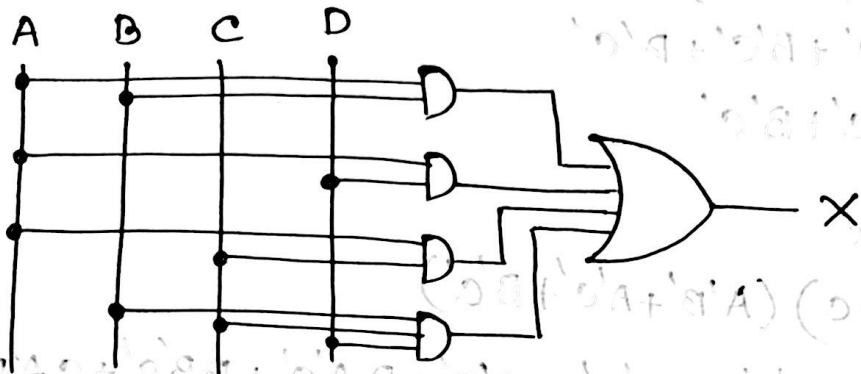

□ Analysis of combinational Circuit:- (Design এর উল্টো)

Analysis:

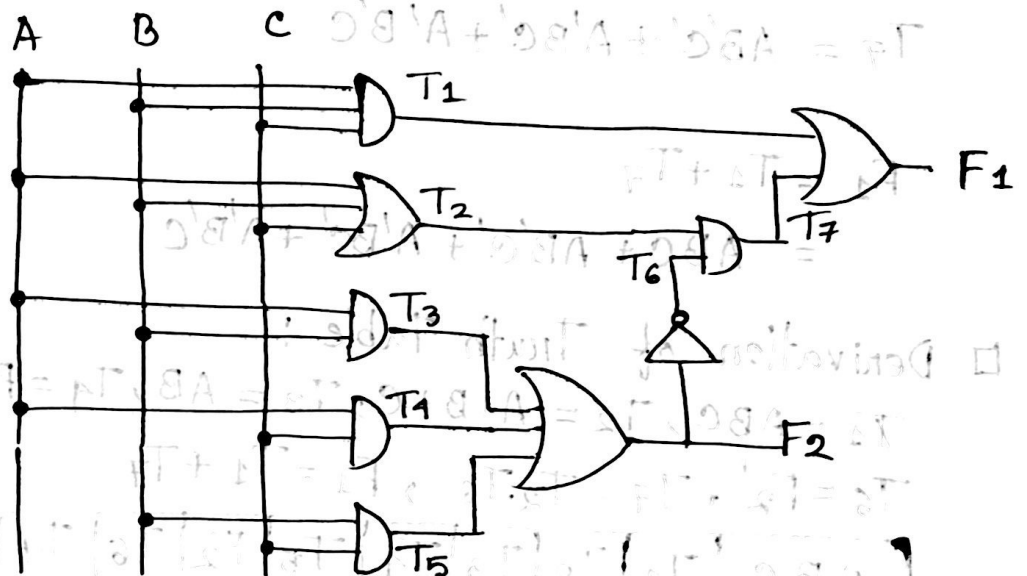

Method-1: Derivation of Boolean Expressions:-

$$T_1 = ABC$$

$$T_2 = A+B+C$$

$$T_3 = AB$$

$$T_4 = AC$$

$$T_5 = BC$$

$$F_2 = T_3 + T_4 + T_5$$

$$F_2 = AB + AC + BC$$

$$T_6 = F_2'$$

$$= (AB + AC + BC)'$$

$$= (AB)'. (AC)'. (BC)'$$

$$= (A'+B')(A'+C')(B'+C')$$

$$= (A' + A'C' + A'B' + B'C')(B'+C')$$

$$= (A'(1+C'+B') + B'C')(B'+C')$$

* কোনো gate এর output থেকে অন্য gate এর input এ গেলে তাকে wine ধরবে

$$= (A' + B'C')(B' + C')$$

$$= A'B' + A'C' + B'C' + B'C'$$

$$T_6 = A'B' + A'C' + B'C'$$

$$T_7 = T_2 \cdot T_6$$

$$= (A + B + C)(A'B' + A'C' + B'C')$$

$$= \underbrace{AA'B'}_0 + \underbrace{AA'C'}_0 + ABC' + \underbrace{BA'B'}_0 + \underbrace{BA'C'}_0 + \underbrace{BB'C'}_0 + \underbrace{CA'B'}_0 + \underbrace{CA'C'}_0 + \underbrace{CB'C'}_0$$

$$= AB'C' + A'BC' + A'B'C$$

$$T_7 = AB'C' + A'BC' + A'B'C$$

$$F_1 = T_1 + T_7$$

$$= ABC + AB'C' + A'BC' + A'B'C$$

□ Derivation of Truth Table :

$$T_1 = ABC, T_2 = A + B + C, T_3 = AB, T_4 = AC, T_5 = BC$$

$$T_6 = F_2', T_7 = T_2 \cdot T_6, F_1 = T_1 + T_7$$

ABC	T ₁	T ₂	T ₃	T ₄	T ₅	F ₂	T ₆	T ₇	F ₁
000	0	0	0	0	0	0	1	0	0
001	0	1	0	0	0	0	1	1	1
010	0	1	0	0	0	0	1	1	1
011	0	1	0	0	1	1	0	0	0
100	0	1	0	0	0	0	1	1	1
101	0	1	0	1	0	1	0	0	0
110	0	1	1	0	0	1	0	0	0
111	1	1	1	1	1	1	0	0	1

Quiz - Chapter 3, Analysis