

Course: CSE345 Digital Logic Design

Expt No.: 3

Title: Behavioral Verilog Simulation of a Combinational Logic Circuit

Objectives:

1. To learn behavioral Verilog coding of a combinational logic circuits using procedural model.
2. To learn behavioral Verilog coding of a combinational logic circuits using continuous assign statement.

Introduction:

The Boolean expression of the combinational logic circuit of Figure 1 is $S = A'B + AB'$. The behavioral Verilog code for the combinational logic circuit of Figure 1 using the procedural model is as follows:

```
module expt3_1 (input A, B,
                output reg S);
    always @(A, B) begin
        S=0;
        if(~A & B) S=1;
        if(A & ~B) S=1;
    end
endmodule
```

The behavioral Verilog code for the combinational logic circuit of Figure 1 using continuous assign statement is as follows:

```
module expt3_2 (input A, B,
                output S);
    assign S = (~A & B) | (A & ~B);
endmodule
```

 


Figure 1: Example of a combination logic circuit.

See Section 14.3 of Textbook 1 for more details.

Pre-Lab Report Question:

1. Write behavioral Verilog code for the combinational logic circuit of Figure 2 using procedural model.
2. Write behavioral Verilog code for the combinational logic circuit of Figure 2 using continuous assign statement.

 


Figure 2: Combinational circuit for lab practice.

Lab Procedure:

1. Simulate both the Verilog codes from your pre-lab report using Quartus II software. Get printouts of Verilog codes and simulation outputs of both the cases in a single page and have it signed by your instructor.

Post-Lab Report Question:

1. Prepare the truth table of the combinational circuit of Figure 2.
2. Compare whether the simulation results agree with the truth table prepared in step 1.