

Exercise

6.9 Analyze the two-output combinational circuit shown in Figure 6.25.

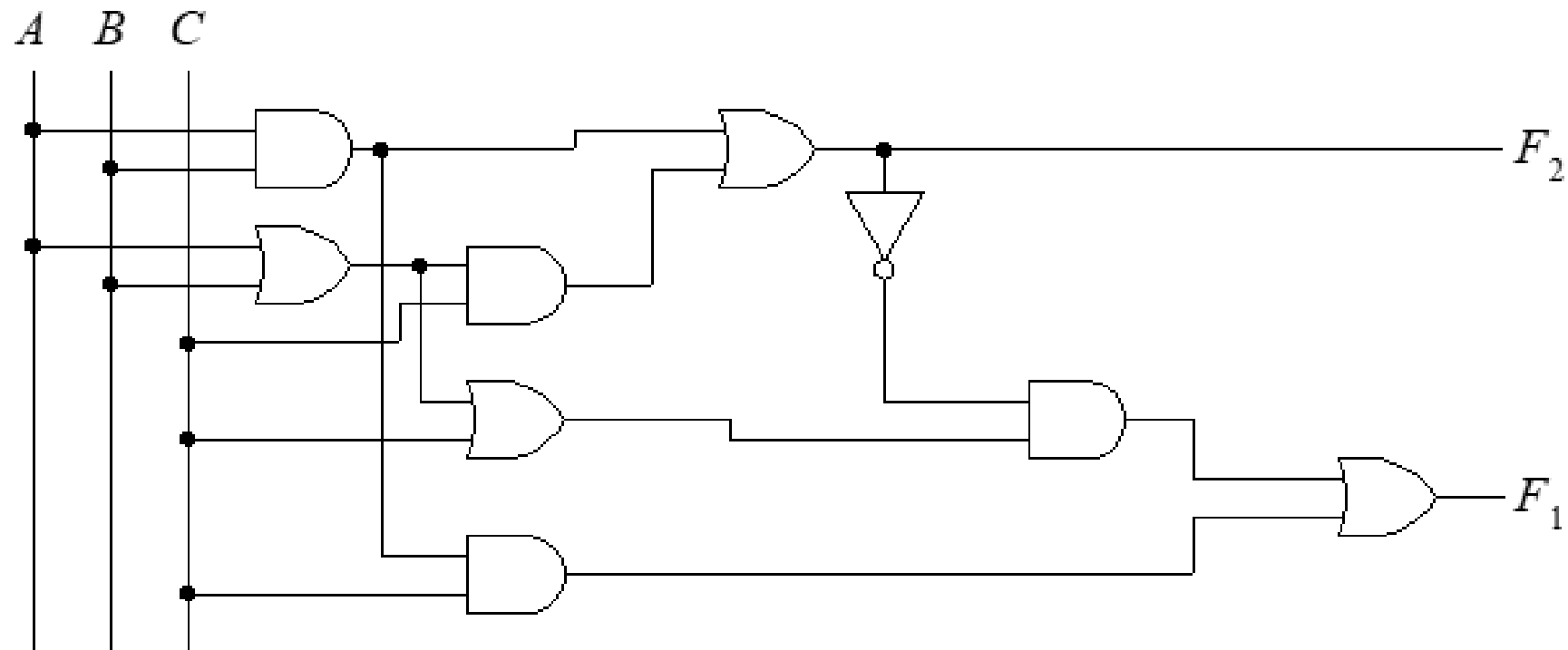


Figure 6.25 Logic diagram for analysis problem 6.9.

Exercise

6.21 Design AND-OR circuits for the following functions

(a) $F(A, B, C, D) = \sum (0, 1, 8, 11)$

(b) $F(A, B, C, D) = \sum (1, 2, 4, 7, 9, 10, 13, 14)$

(c) $F(A, B, C, D) = \sum (0, 1, 3, 6, 7, 8, 10, 13)$

(d) $F(A, B, C, D) = \sum (0, 1, 2, 3, 8, 11)$

(e) $F(A, B, C, D) = \sum (0, 1, 3, 6, 7, 8, 11)$