

1. Design a sequential circuit represented by the following transition table using T Flip-Flop.  
[CO3, Mark: 05]

Present State $Q_1 Q_2$	Next State $Q_1 Q_2$		Output, $z$		Flip-Flop Inputs			
	$Q_1 Q_2$				$T_1 T_2$		$T_1 T_2$	
	$x=0$	$x=1$	$x=0$	$x=1$	$x=0$	$x=1$	$x=0$	$x=1$
00	00	10	1	1	0	0	1	0
01	11	01	0	1	1	0	0	0
11	11	10	0	0	0	0	0	1
10	01	11	1	1	1	1	0	1

$T_1$ :

$Q_1 Q_2$	$x=0$	$x=1$
00	0	1
01	1	0
11	0	0
10	1	0

$$T_1 = Q_1' Q_2 x' + Q_1 Q_2' x' + Q_1' Q_2' x$$

$T_2$ :

$Q_1 Q_2$	$x=0$	$x=1$
00	0	0
01	0	0
11	0	1
10	1	1

$$T_2 = Q_1 Q_2' + Q_1 x$$

$z$ :

$Q_1 Q_2$	$x=0$	$x=1$
00	1	1
01	0	1
11	0	0
10	1	1

$$z = Q_2' + Q_1 x$$