

CSE345 Digital Logic Design

Course Outcome: CO4

Program Outcome: PO3

Cognitive Level: C3

Psychomotor Level: P2, P3

Affective Level: A2

Knowledge Profile: K4, K5

Complex Engineering Problem: EP1, EP2

Project-1

3-Input Majority Detector

Design and implement a combinational circuit that detects the majority value (1s or 0s) among three binary inputs. The circuit outputs LOGIC HIGH (1) only when two or more inputs are 1- indicating a majority of 1s.

Project-2

3-Bit Binary to Gray Code Converter

Design and implement a 3-bit binary to Gray code converter using logic gates. The circuit converts standard binary numbers to Gray code, where only one bit changes at each transition.

Marks Distribution

Assessment Area	Mark
C3: Cognitive: Applying	7
P2: Psychomotor: Manipulation	1
P3: Psychomotor: Precision	1
A2: Affective: Responding	1
Total	10

Project Report will include

1. Problem Statement
2. Design Details
3. Circuit Diagram
4. Behavioral Verilog Code (Procedural Model and Continuous assign Statement) and Simulation Result (Screenshots)

Note: Odd digit will undertake Project-1 and Even digit will undertake Project-2.