



EAST WEST UNIVERSITY

Department of Computer Science and Engineering

B.Sc. in Computer Science and Engineering Program


Mid Term II Examination, Fall 2021 Semester

Course: CSE 345 Digital Logic Design, Section-2
Instructor: Musharrat Khan, Senior Lecturer, CSE Department
Full Marks: 40 (20 will be counted for final grading)
Time: 1 Hour and 25 Minutes (Including Submission)

Note: There are SIX questions, answer ALL of them. Course Outcome (CO), Cognitive Level and Mark of each question are mentioned at the right margin.

1. Consider that $ABCD$ are 4-bit inputs and X is 1-bit output of a combinational circuit. The output is $X = 1$ if the sum of the four inputs is greater than or equal to 2; otherwise $X = 0$. **Design** the combinational circuit. [CO3,C3, EP1,EP2, Mark: 6]

 2. **Analyze** the following circuit by writing the Boolean expression of the outputs. [CO2,C4, EP1, Mark: 8]



3. **Design** a full-adder using only AND, EXOR, and OR gates. [Draw block diagram, construct truth table, determine Boolean equations of outputs, and draw logic diagram] [CO3,C3, Mark: 6]
4. **Design** a 4×16 Decoder for active-LOW outputs. [Draw block diagram, construct truth table, determine Boolean equations of outputs, and draw logic diagram] [CO3,C6, Mark: 6]

5. **Construct** a combinational circuit using an 8×1 MUX for implementing the following Boolean function. [Properly label all the inputs and outputs]

[CO3,C6,
EP1,EP2,
Mark: 6]

$$F(A, B, C, D) = \prod (1, 4, 6, 7, 10, 12, 15)$$

6. **Write** a behavioral Verilog code to design the following Boolean function using Procedural technique using case statement.

[CO3,C6,
EP1,EP2,
Mark: 8]

$$F(A, B, C, D) = (A + D')C' + (B' + D)$$